



RPC Front End & Synchronization



- **RPC signal characteristics and FE electronics requirements**
- **FE electronics layout for synchronization**
- **Sources of RPC signal timing indetermination**
- **Results on last test beam data**
- **Results on laboratory FE board tests (Synchronizer)**
- **Conclusions: New Front End Chip & new FEB implementation**




RPC



Shape of the signal: $I(t) = I_0 \exp(t/\tau)$ ($0 \leq t \leq 15$ ns)

 $\tau = 1/\eta v$ (~ 0.8 ns, at detector working point)



Strip line 1.3 m long and 2 - 4 cm wide:

$$15 \Omega \leq R_0 \leq 40 \Omega$$

$$160 \text{ pF} \leq C_{\text{strip}} \leq 350 \text{ pF}$$

Propagation delay ~ 5.5 ns/m

- **Input dynamic range:** $20 \text{ fC} \leq Q_{\text{in}} \leq 20 \text{ pC}$
- **Expected rate:** $< 400 \text{ KHz}$

RPC Front-End chip (1997-1998)




- Shape of the signal: $I(t) = \exp(t/\tau)$ ($0 \leq t \leq 15$ ns)
- Strip line 1.3 m long and 2-4 cm wide:
 - $15 \Omega \leq R_0 \leq 40 \Omega$
 - $160 \text{ pF} \leq C_{\text{strip}} \leq 350 \text{ pF}$
 - Propagation delay ≈ 5.5 ns/m
- Input dynamic range: $20 \text{ fC} \leq Q_{\text{in}} \leq 20 \text{ pC}$

The circuit

Six channels, each one consisting of:

 - charge amplifier
- leading-edge discriminator
- one-shot
- differential line driver



Amplifier characteristic:


- Current sensitive preamplifier:
 - $R_{\text{in}} = 30 \Omega$ at the signal frequencies (100 MHz)
 - Dominant pole ~ 180 MHz
- Gain stage:
 - Dominant pole ~ 18 MHz
 - Charge sensitivity $\sim 1.6 \text{ mV/fC}$
 - Power consumption $\sim 7 \text{ mW}$
 - ENC_{TOT} (strip connected and terminated) $\leq 1.6 \text{ fC}$

Discriminator + One-shot characteristics:

- $10 \text{ fC} \leq Q_{\text{th}} \leq 300 \text{ fC}$
- $70 \text{ ns} \leq T_{\text{W}} \leq 200 \text{ ns}$
- Power consumption $\sim 7 \text{ mW}$

Output stage characteristics:

 - Output Voltage swing: 0-300mV
- $R_0 = 110 \Omega$
- 5 mW (high impedance) \leq Power consumption $\leq 17 \text{ mW}$ (110Ω)





RPC Front_End board components




(1998 Test Beam implementation)

- **Modularity: 12 channels**
- **Front_End chip (Amplifier, Discriminator, One_Shot, Driver)**
- **Front_End Control Electronics:**
 - **DAC** (threshold settings, 1.2 fC resolution)
 - **FIFO** for test pattern (512 x 18 bit word)
 - **Synchronization Unit** (window: position and width)
 - **40 MHz clock**
- **LVDS output driver**
- **NIM module for remote control (present implementation)**



RPC




RPC Fron End Board Layout (1998)

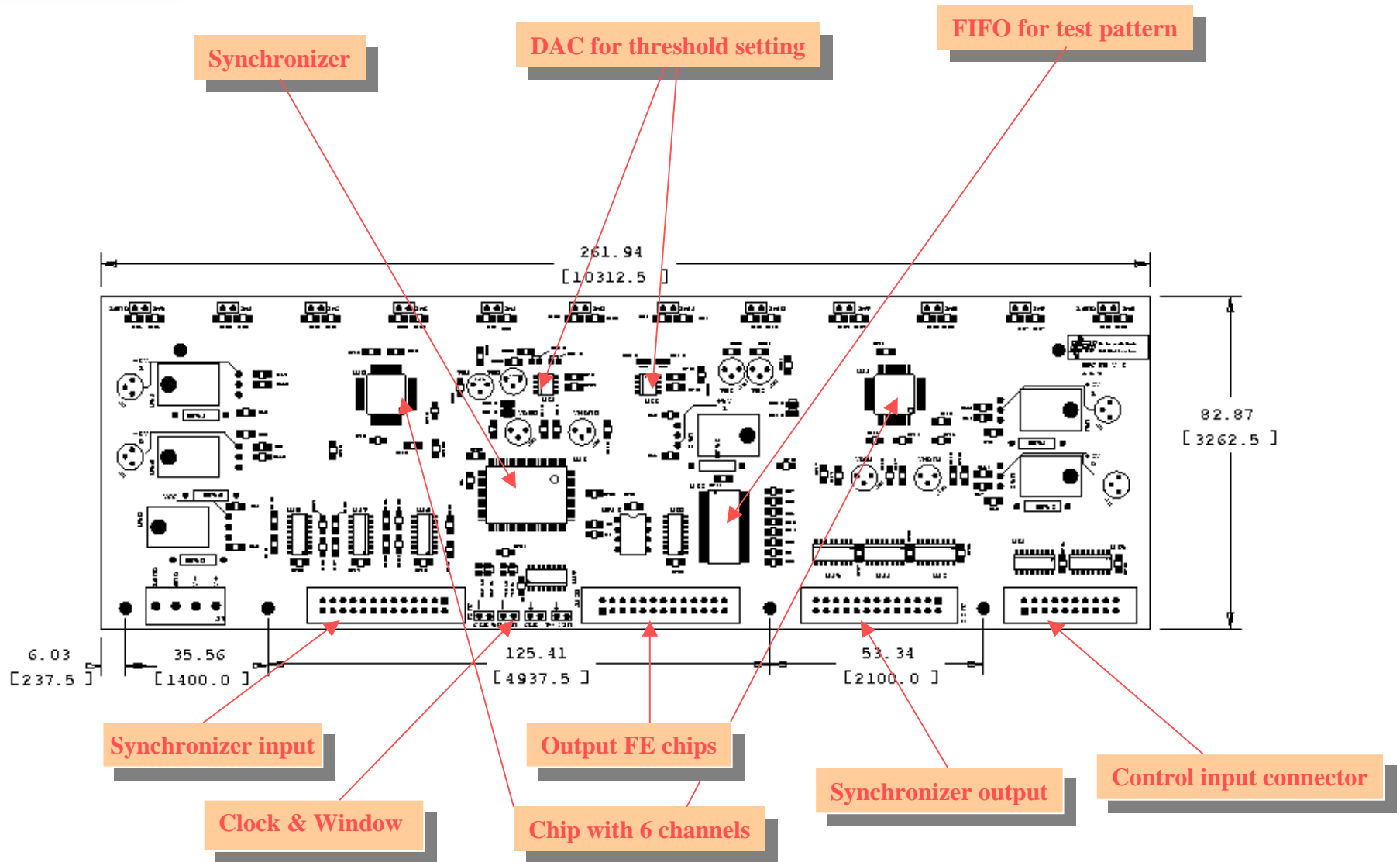



RPC

RPC Front End & Synchronization Layout

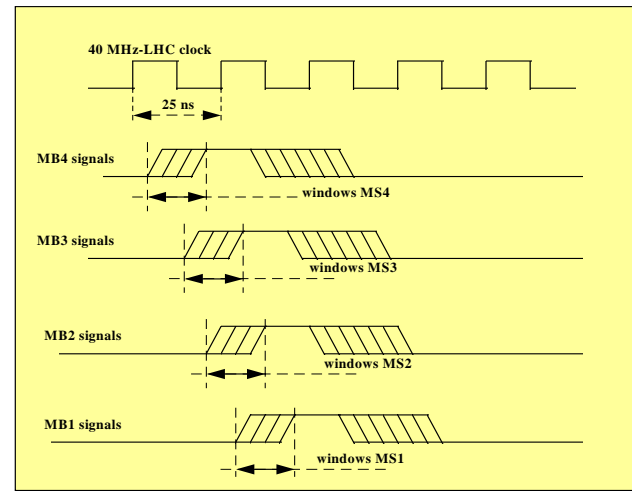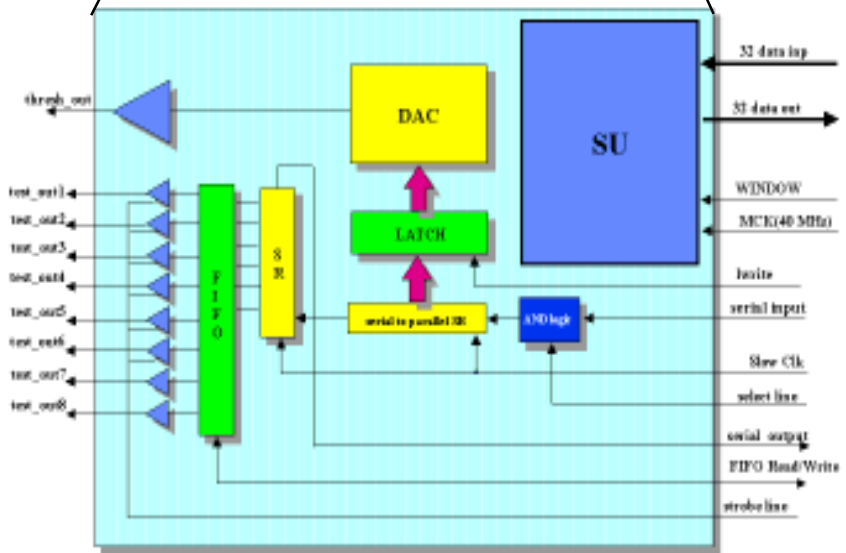
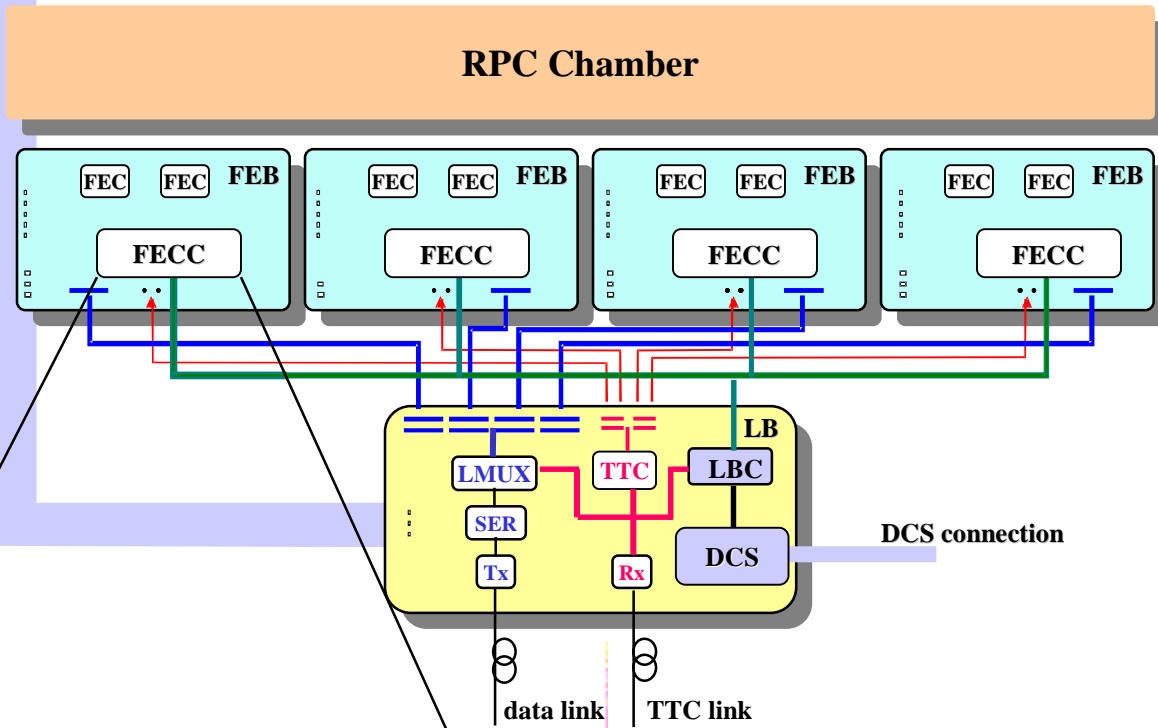




RPC

Alignment of RPC signals


required precision: ~ 1 ns

 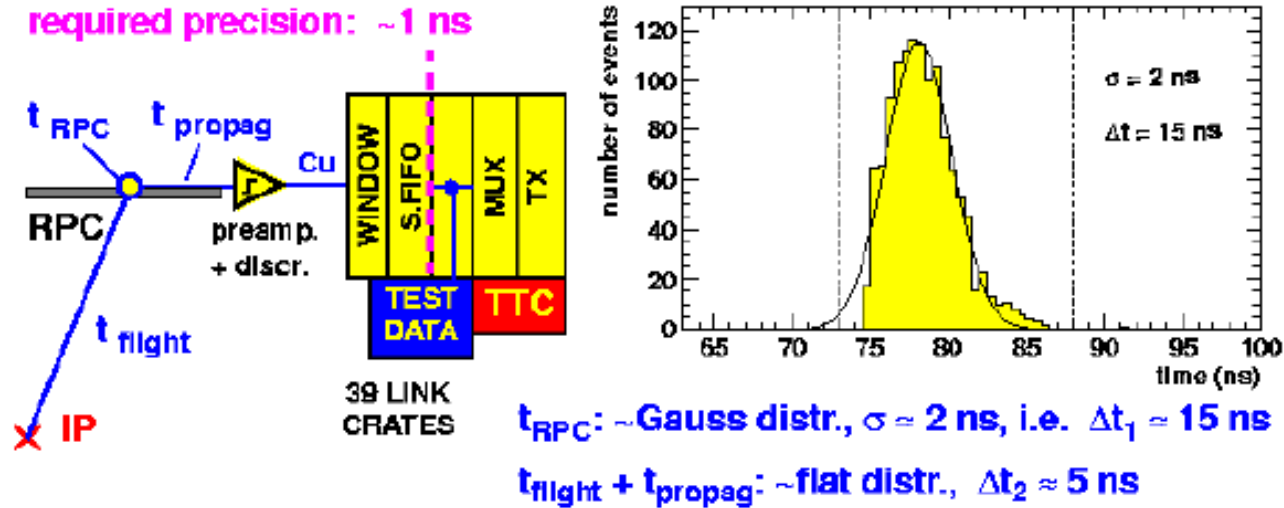



RPC

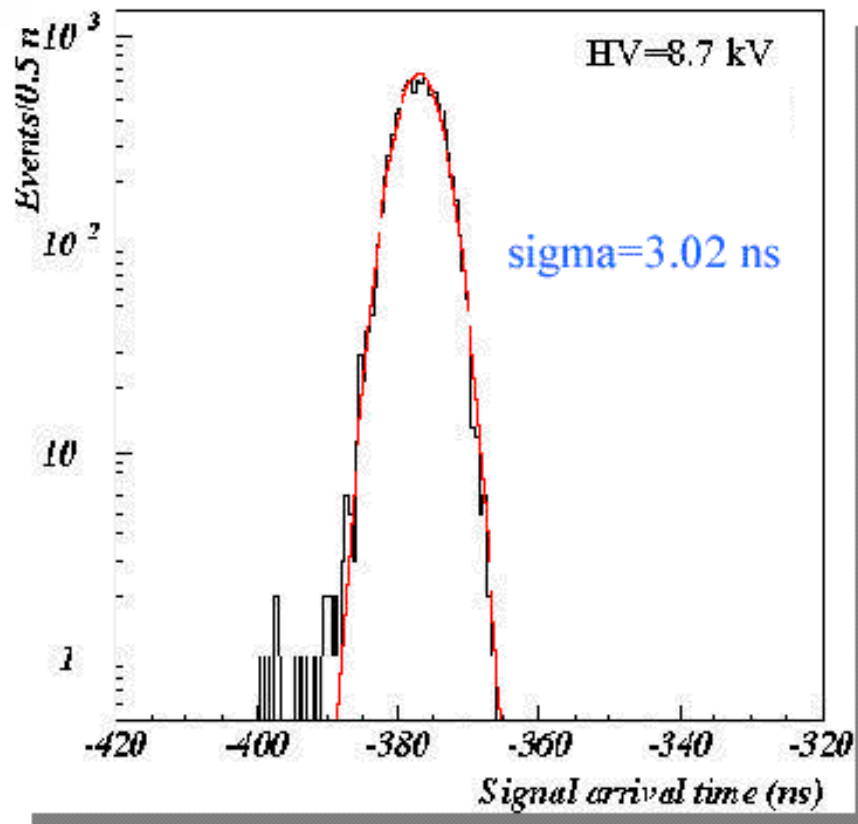Signal arrival time distribution (arbitrary zero)



The tail on the left hand side is consistent with the background due to the spurious.

CMS Note 1998/0000

6th International Conference on
Advanced Technology and Particle Physics
Villa Olmo, October 5-9, 1998


CMS Synchronization Workshop, CERN November 11, 1998

A. Ranieri INFN Bari



Corrected signal arrival time distribution for a 2 mm RPC

CMS Note 1998/0000


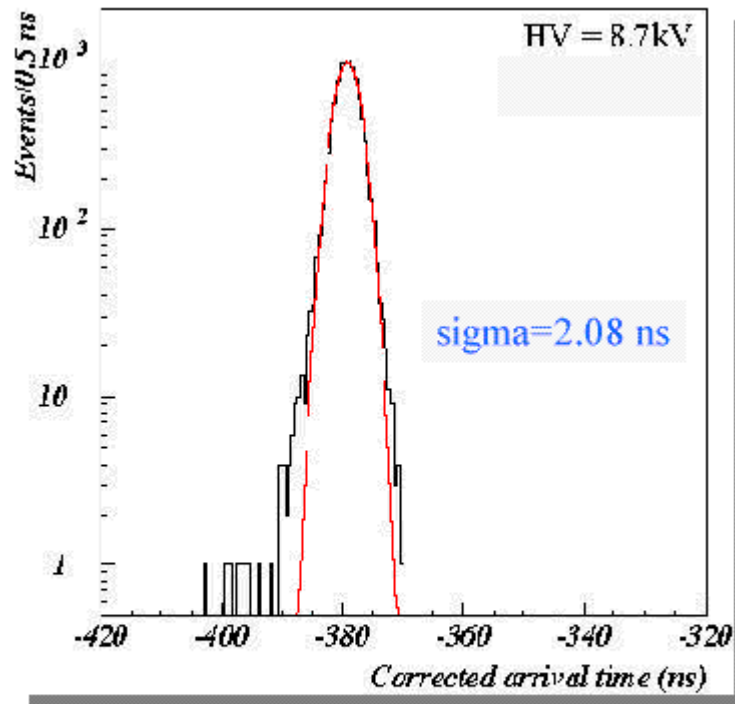


Correction for different signal propagation time along the read-out strips is taken into account by subtracting the time needed by each signal to reach the front-end board (a signal speed of 0.66 c is assumed).

Sigma improves from ~ 3 ns to ~ 2 ns

6th International Conference on
Advanced Technology and Particle Physics
Villa Olmo, October 5-9, 1998

  
Chamber efficiency as a timing window function





RPC


CK & WIN generation test circuit

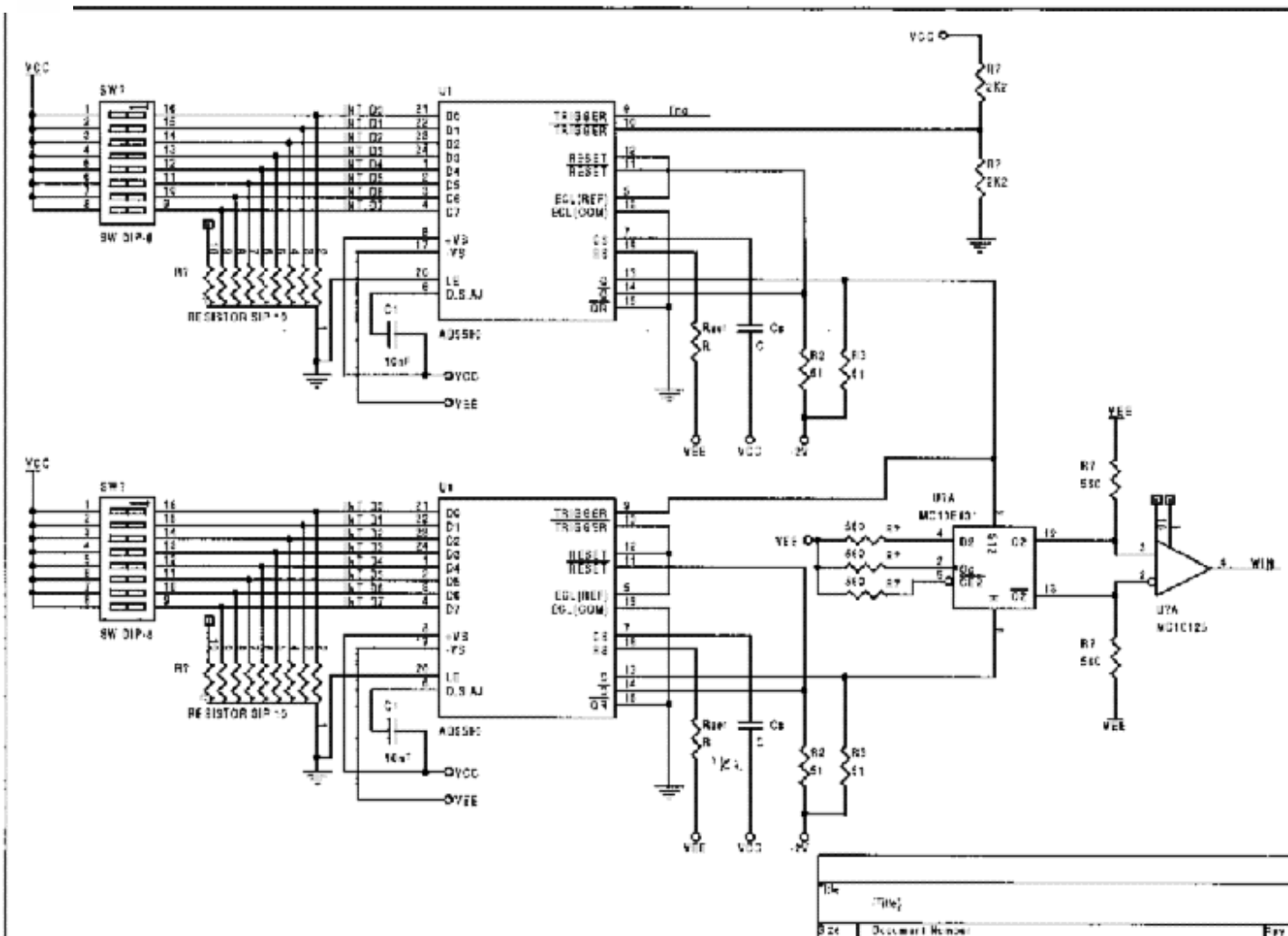



RPC

FE board amplifier output

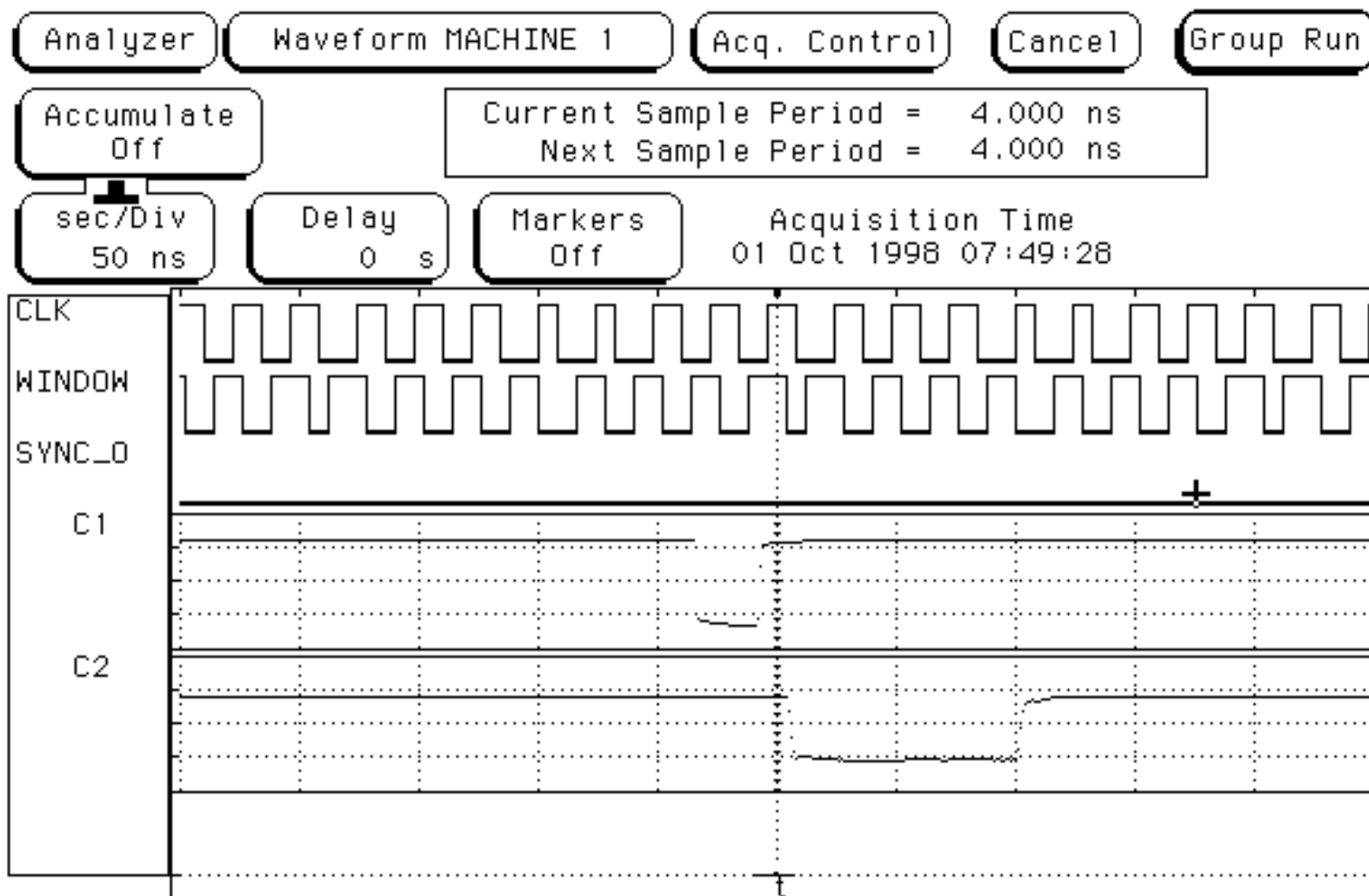




RPC

hp

Synchronizer test circuit output

 



RPC

NEW FRONT END CHIP FOR RPC DETECTOR OF CMS



- **Charge preamplifier for strip impedance matching (15-30 Ω)**
- **AC - coupling with discriminator for low offset (< 3 fC) and low dead time (< 70 ns)**
- **Zero - crossing discriminator for amplitude - independent timing response (< 3 ns)**
- **One - shot with tunable pulse width**
- **Low - voltage differential line driver (LVDS compatible) with tunable output current**
- **The FE chip will contain 8 channels**
- **developed in 0.8 μ BiCMOS technology by AMS**
- **Foundry run 4 December through CMP**



Front_End Board Control components



1999 implementation (not final)

- **The Front_End Board will contain 16 RPC channels**
- **Two 10-bit CMOS DAC's with 2.5 V reference voltage & with very low power consumption (3 mW)**
- **Discriminator threshold resolution: 1.2 fC/bit**
- **Low Power CMOS clocked FIFO operating @ 3.3 V, as test pattern generator for the 16 RPC channels**
- **Injected charge for test pattern: 660 fC (**discriminating capability: $10 \text{ fC} < Q_{th} < 300 \text{ fC}$**)**
- **Synchronization Unit for the 16 RPC channels controlled by the system Clock (@ 40 MHz) and a Window pulse, with adjustable phase respect to the Clock (feed from external)**
- **OR8 (OR16) functions & histogramming capability integrated in the SU**
- **The various components will be remotely controlled by LB**
- **LVDS output driver**